

Digital Design – Combinational Logic II


Dr. Ipsita Biswas Mahapatra
Member of Technical Staff

Goals & objectives

- Multiplexers
- De-multiplexers
- Encoders
- Decoders
- Priority encoders
- Comparator
- Half adder, Full adder
- Half subtractor, Full subtractor


Multiplexers

- It has two data inputs, one data output, and a select input that determines which input value is used for the output value.
- We can expand on this simple multiplexer along two dimensions:
 - First, we can add more data inputs, which also requires adding further select inputs to encode the choice of input to drive the output.
 - Second, we can use multiplexers in parallel to select between two sources of multibit encoded data.

 


- N-to-1 multiplexer needs $\lceil \log_2 N \rceil$ select bits

Multiplexer as data selector

 

Multiplexer – with 2 control signals


 


E	S	Y
0	X	0
1	0	I_0
1	1	I_1






$$Y = E.S'.I_0 + E.S.I_1$$

Multi-bit Multiplexers

 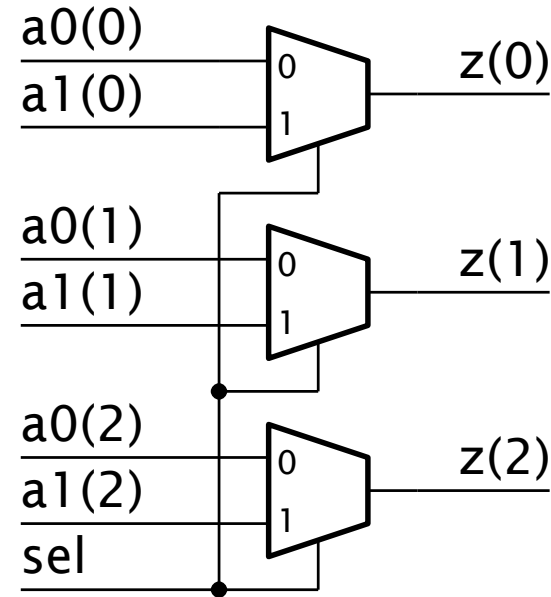- To select between N m -bit codeword inputs
 - Connect m N -input multiplexers in parallel
- Abstraction
 - Treat this as a component






Basic gates using 2:1 Mux

     


De-multiplexer

 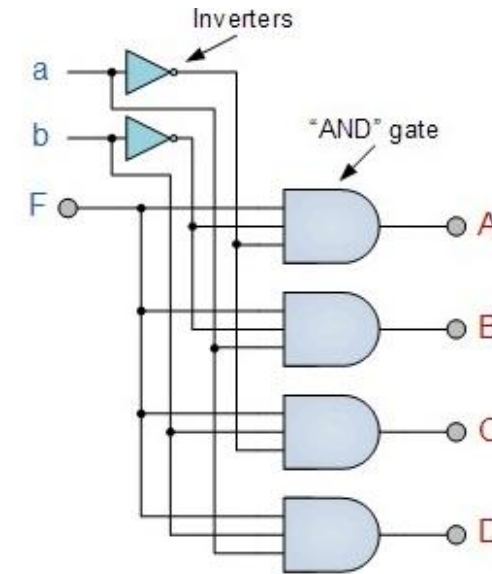 - Used to connect a single source to multiple destinations.
- Example – Drive same signal to various outputs based on the selection.




Input	Select Lines	Output Lines
I	S ₁ S ₀	D ₀ D ₁ D ₂ D ₃
I	0 0	1 0 0 0
I	0 1	0 1 0 0
I	1 0	0 0 1 0
I	1 1	0 0 0 1

De-multiplexer

 

Select Inputs		Input	Data Outputs			
b	a	D	Y_3	Y_2	Y_1	Y_0
0	0	1	0	0	0	1
0	1	1	0	0	1	0
1	0	1	0	1	0	0
1	1	1	1	0	0	0
 
$$D = \overline{a}\overline{b}Y_0 + a\overline{b}Y_1 + \overline{a}bY_2 + abY_3$$




Summary: Mux and De-mux


- Mux
 - It is a combinational circuit that selects binary information's from one of many input lines and direct it to output line
 - It is simply a data selector
- De-mux
 - One input many outputs
 - Data distributors
 - Reverse operation of mux

Encoder

 - Applications: Decimal to Binary encoding in calculators
 - Required only one bit of all the input bits to be 1
 - If this is violated; then the output is 0



INPUTS				OUTPUTS	
Y3	Y2	Y1	Y0	A1	A0
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1

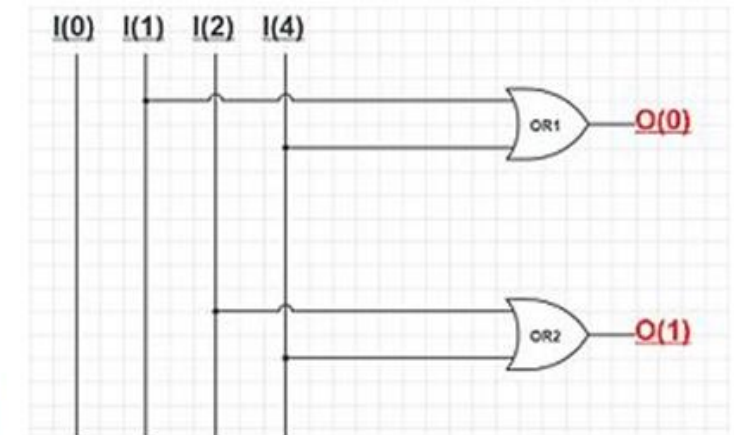



Priority Encoders

- Now let's consider the possibility of more than one input to an encoder being 1 at a time. The design we described above would produce an incorrect output, possibly an invalid code word.
- The solution is to assign priorities to the inputs, so that if multiple inputs are 1, the encoder outputs the code word corresponding to the input with highest priority.
- Such an encoder is called, not surprisingly, a priority encoder .
- One application of priority encoders is to prioritize interrupts in embedded systems.

Priority encoder

- Applications: Decimal to binary encoding in calculators
 - Special type of encoders whose output corresponds to the currently active input, which has the highest priority. So, when an input with a higher priority is present, all other input with lower priority will be ignored.

Inputs				Outputs		
D ₀	D ₁	D ₂	D ₃	Y ₁	Y ₀	V
0	0	0	0	×	×	0
1	0	0	0	0	0	1
×	1	0	0	0	1	1
×	×	1	0	1	0	1
×	×	×	1	1	1	1

  


Decoders

- Information's are mostly binary coded.
- In many designs, we need to derive a number of control signals from a binary coded signal, with one control signal corresponding to each valid code word.
- When the encoded signal takes on a given code value, the corresponding control signal is activated. We call a circuit that derives the control signals in this way a decoder.
- For an n-bit code, if every code word is valid, the decoder will have 2^n outputs.

Decoder


 
- Usage example: Traffic light controller




A 2-to-4 decoder without enable

Decimal #	Input		Output			
	A ₁	A ₀	D ₀	D ₁	D ₂	D ₃
0	0	0	1	0	0	0
1	0	1	0	1	0	0
2	1	0	0	0	1	0
3	1	1	0	0	0	1

Truth table for 2-to-4 decoder

  

 

Comparator


a	b	a=b	a>b	a<b
0	0	1	0	0
0	1	0	0	1
1	0	0	1	0
1	1	1	0	0

$$a=b: a'b' + ab$$

$$a>b: ab'$$

$$a<b: a'b$$

 
The logic for $a=b$ is also: $(a'b + ab')'$




2-Bit Comparator truth table

Inputs				Outputs		
A ₁	A ₀	B ₁	B ₀	A>B	A=B	A<B
0	0	0	0	0	1	0
0	0	0	1	0	0	1
0	0	1	0	0	0	1
0	0	1	1	0	0	1
0	1	0	0	1	0	0
0	1	0	1	0	1	0
0	1	1	0	0	0	1
0	1	1	1	0	0	1
1	0	0	0	1	0	0
1	0	0	1	1	0	0
1	0	1	0	0	1	0
1	0	1	1	0	0	1
1	1	0	0	1	0	0
1	1	0	1	1	0	0
1	1	1	0	1	0	0
1	1	1	1	0	1	0


2-bit comparator

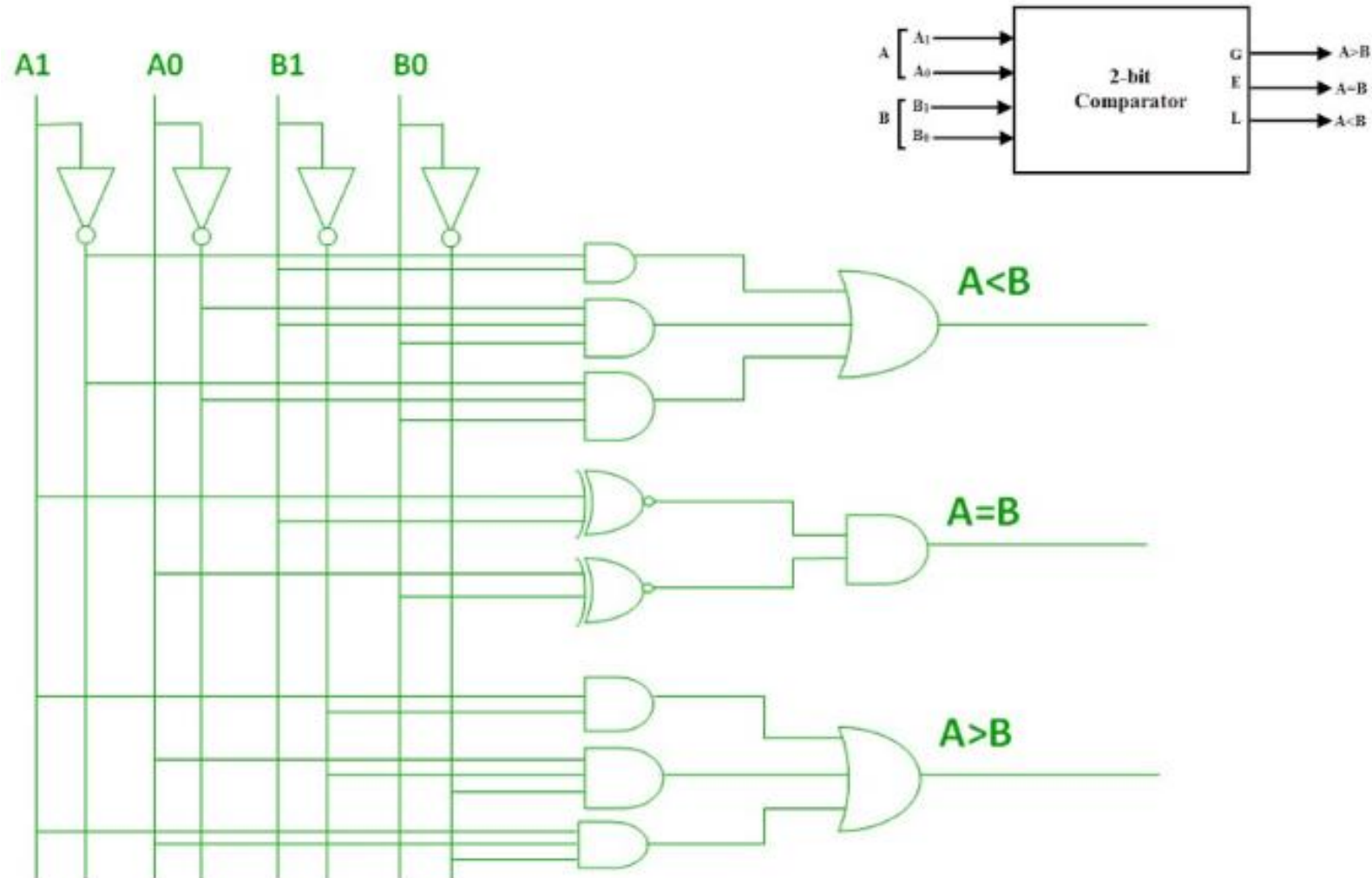


Half adder

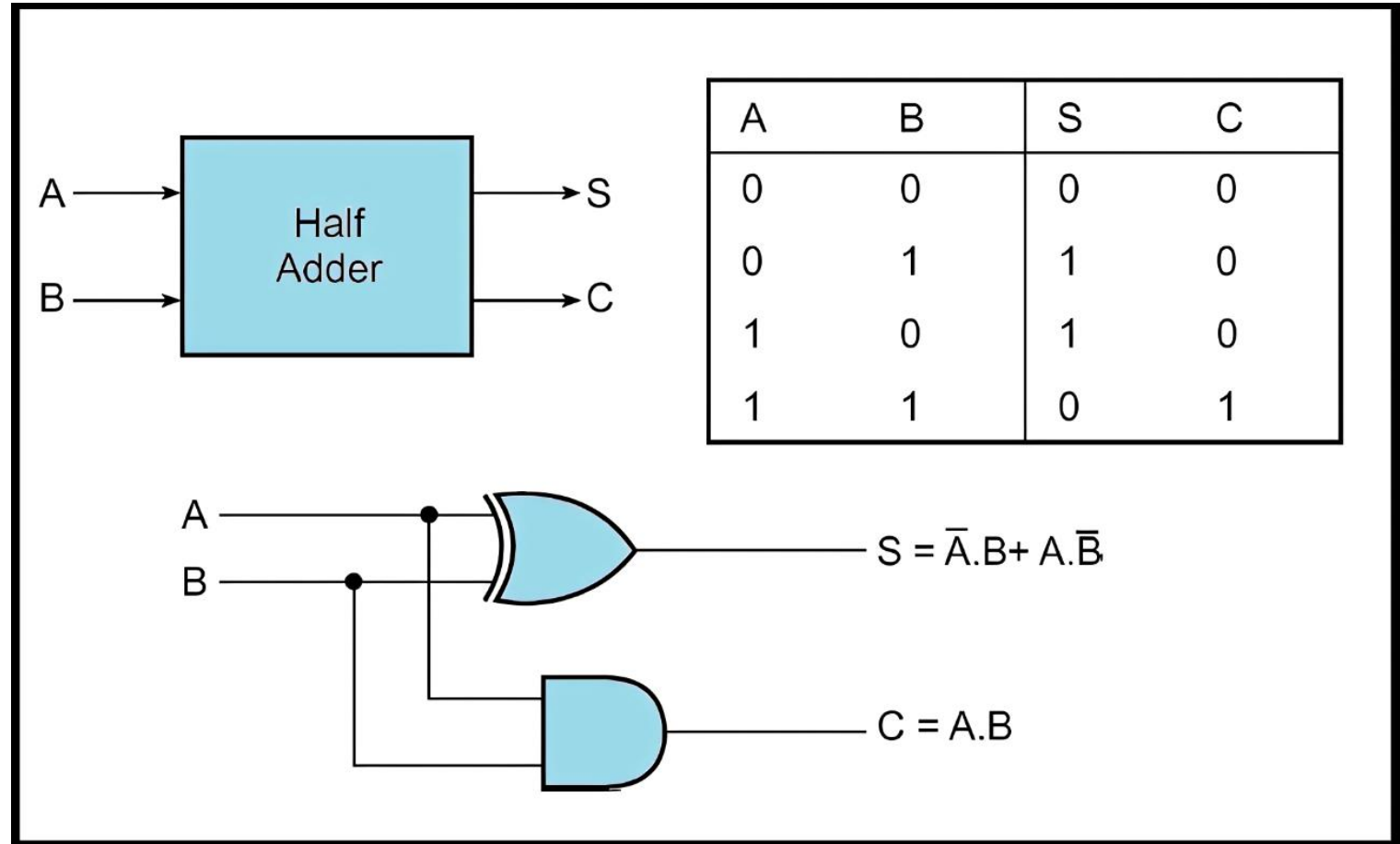

Half adder – using NAND gates

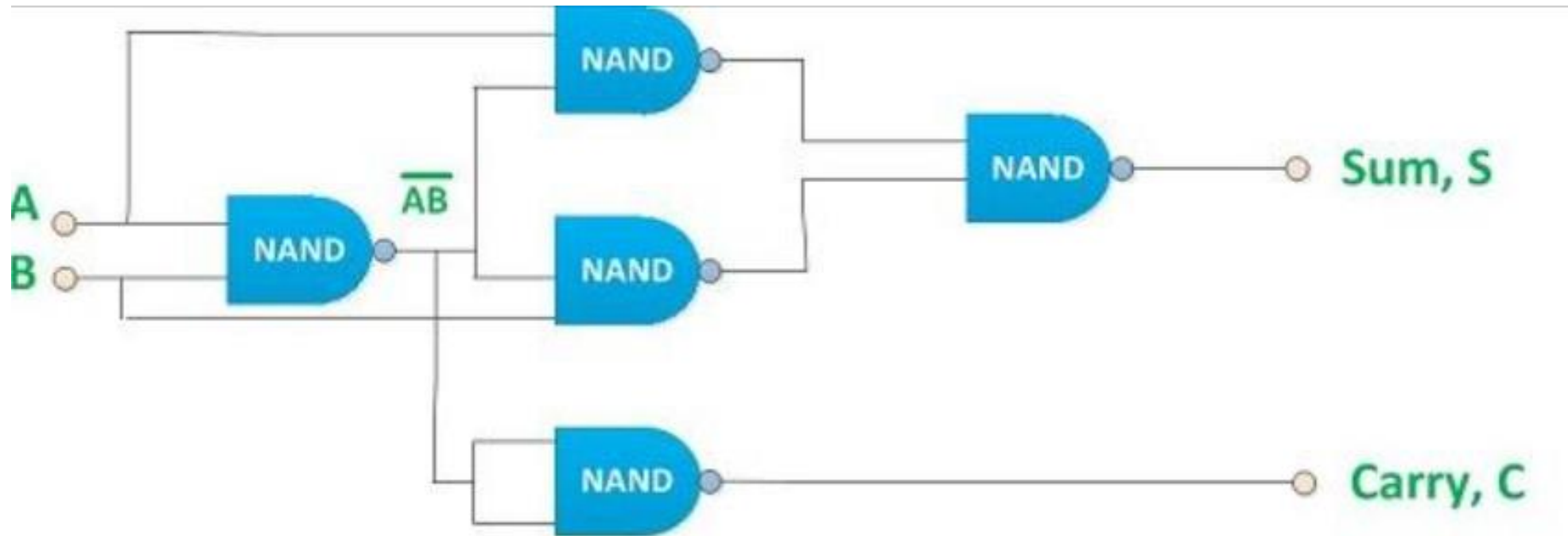


Full adder

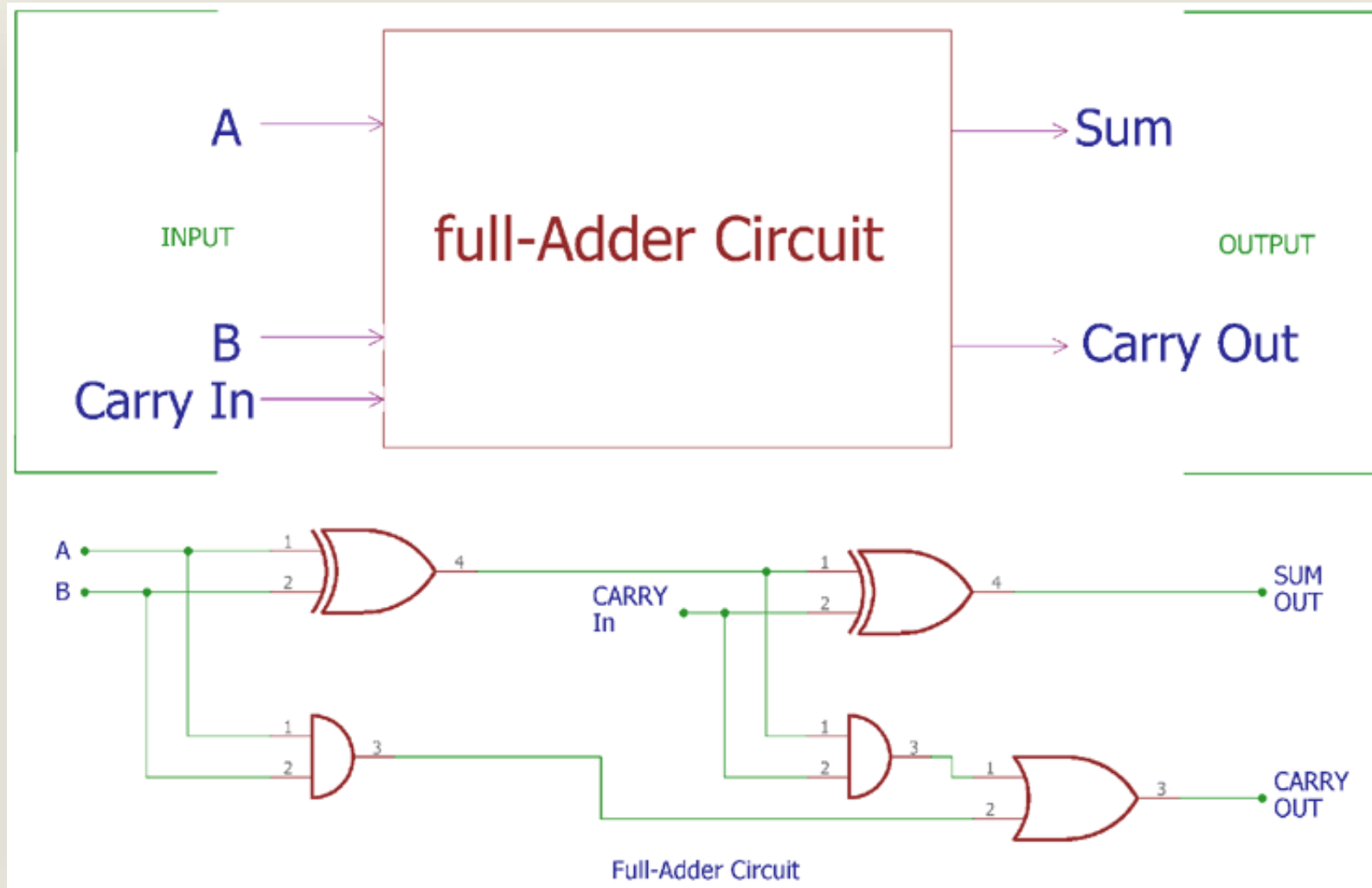


Inputs			Outputs	
A	B	Cin	Sum	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Full-adder using Half-adder

 


4-bit full-adder using 1-bit full-adder

 The number of full adder will be equal to the number of bits; in this number of bits is 5 so we need 5 full adders (FA)




4-bit full-adder using 1-bit full-adder

 


Full-adder using NAND gate

Full-adder using NAND gate

 


Full-adder using NOR gate


Full-adder using NOR gate

 



Half-subtractor

 

Inputs		Outputs	
X	Y	D	B
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

 


Full-subtractor

  


INPUT			OUTPUT	
A	B	Bin	D	Bout
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

Full-subtractor using half-subtractor

 

 
4-bit full
subtractor
using 1-bit
full
subtractor




Agenda

- Full-adder implementation using half-adders
- Full-subtractor implementation using half-subtractor
- Full-adder realisation using NAND and NOR gates
- Full-subtractor realisation using NAND and NOR gates
- Implementing Boolean expression using NAND and NOR gates
- MUX and De-MUX

 
Boolean function implementation using 2x1 Mux



 
Boolean function implementation using 4x1 Mux




Full-adder using 4x1 Mux

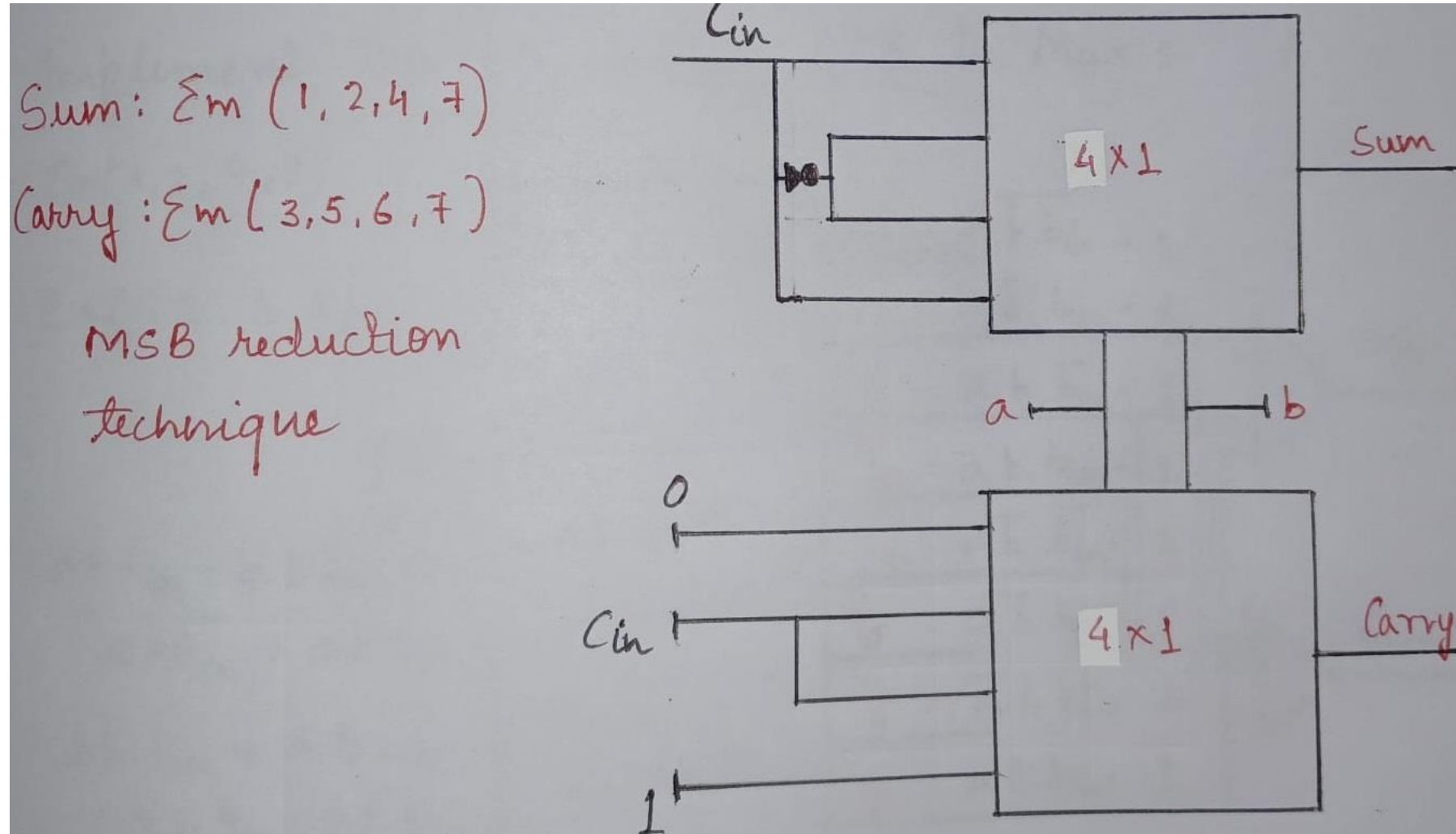

 Representing Boolean expression using a De-mux



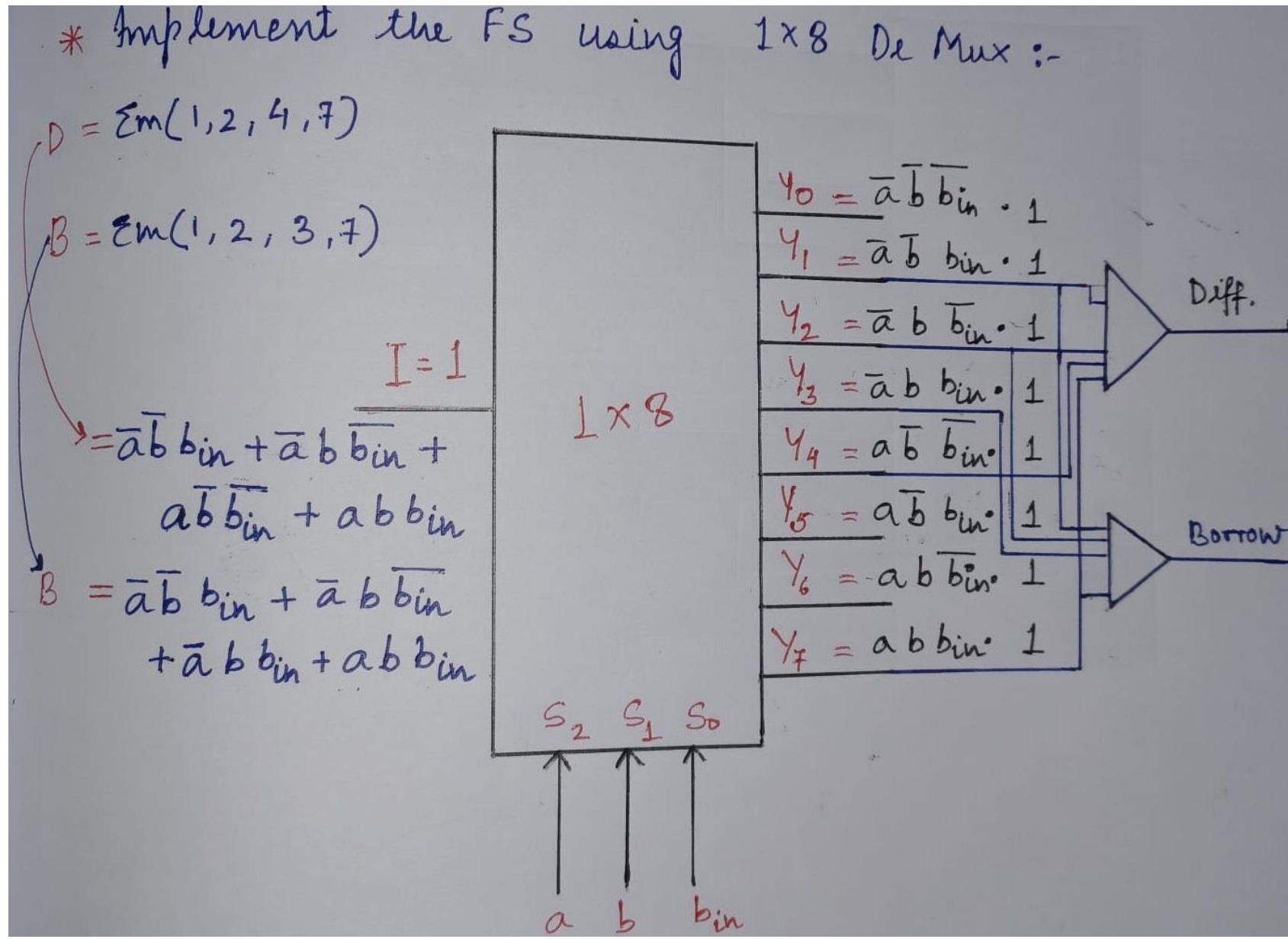Representing a full-subtractor using a De-mux



Hazards in combinational logic

- Both inputs are given to a circuit at the same time, but they arrive at the final gate input at different times, due to the delays added by the gates in the path.
 - This difference in arrival times, create short duration of unwanted glitch at the gate output.
- Both A and B are changed at the same time
 - A = 1 to 0
 - B = 1 to 0
- How to resolve?
 - Use the paths in such a way that both paths have similar delay
 - This can be done using K-map
 - We won't be able to avoid 100% hazards, but they can be minimized.

Thank you

Heading

- Input fields

Problems on NAND and NOR

- Draw the CMOS representation of NAND and NOR gate?
- Implement $y = AB + CD$ using NAND gates
- Implement $(\sim X + \sim Y)(Z + W)$
- Implement $(\sim A + B)C + \sim F + DE$ using NAND and NOR gates
- Implement $A\sim BC$ using 2-input NAND gates

Problems based on universal gates

- Implement $y=AB+CD$ using NAND gates?
- Implement $(\sim x + \sim y)(z+w)$?
- Implement $(\sim A+B)C + \sim F + DE$ using NAND and NOR gates?
- Implement $A\sim BC$ using 2 input NAND gates?
- Realisation of full-subtractor using NAND and NOR gates.
- $F(A,B,C) = (A.B.C) + (A'.B') + (A.B'.C) + (A.C')$
 - How to convert this SOP to POS?
- $AB + A\sim C + BC = AB + A\sim C$, optimize this logic?

Multiplexer – Example

```

module mux41(input_lines,select_lines,Y);

[1:0]  select_lines;  // select_lines declared
[3:0]  input_lines;   // input_lines declared
output Y;

reg Y;
wire[1:0]  select_lines;
wire[3:0]  input_lines;

always @(input_lines or select_lines)
    case(select_lines)
        2'b00: Y = input_lines[0];
        2'b01: Y = input_lines[1];
        2'b10: Y = input_lines[2];
        2'b11: Y = input_lines[3];
    endcase
endmodule

```

Combinational logic-based questions

- POS \rightarrow SOP conversion and vice-versa
 - Minterms, maxterms \Rightarrow sigma, pie
- POS realisation using Mux
- Decoder realisation using Mux
- 1-bit and 2-bit comparator using Mux
- Full-adder and Half-adder using decoder
- 16x4 encoder realisation using smaller encoders
- Mux implementation using tri-state buffers
- Bigger decoder using smaller decoder
- Bigger Mux using smaller Mux
- Bigger demux using smaller de-mux
- Bigger comparator using smaller comparator
- Bigger full-adder using smaller full-adder




Problems based on Mux and De-Mux

- Implement 4x1 Mux using 2x1 Mux
- Implement 8x1 Mux using 2x1 Mux
- Implement 8x1 Mux using 4x1 Mux
- Implement 5x1 Mux using 2x1 Mux
- Implement full-adder using 4x1 Mux
- Implement 16x1 Mux using 4x1 and 2x1 Mux
- Implement 32x1 Mux using 8x1 and 4x1 Mux
- Implement full-subtractor using 4x1 Mux
- Implement full-adder using 2x1 Mux only

Combinational logic-based questions

- Bigger full-subtractor using smaller full-subtractor
- Min terms realisation using 2:4 decoder
- Max-term realisation using 2:4 decoder
- Implement full-adder using de-mux
- Implement full-subtractor using de-mux
- Implement full-adder and half-subtractor using de-mux

Multiplexer

   

Selection Lines		Output
s_1	s_0	Y
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3


- Used to select one among multiple inputs
- Generally used: 2x1, 2x1, 8x1
- Other types also possible: 3x1


Multi-bit Mux Example

```
module multiplexer_3bit_2_to_1 ( output [2:0] z,
                                input  [2:0] a0, a1,
                                input          sel );


    assign z = sel ? a1 : a0;
endmodule
```

Full-adder using 2x1 Mux and XOR

 

 

Full-subtractor using multiplexers

 

Designing Encoders

- We can derive the Boolean equation for each bit of the output by identifying those inputs for which the output bit is 1.
- The output bit is then the logical OR of those inputs.

Example:

- Design an encoder for use in a domestic burglar alarm that has sensors for each of eight zones. Each sensor signal is 1 when an intrusion is detected in that zone, and 0 otherwise. The encoder has three bits of output, encoding the zone as follows:

Zone 1: 000 Zone 2: 001 Zone 3: 010 Zone 4: 011
Zone 5: 100 Zone 6: 101 Zone 7: 110 Zone 8: 111

Designing Encoders – Example

Solution:

- The left-most bit of the output code is 1 when any of the zone 5 through zone 8 inputs is 1, so the equation for that output is the logical OR of those zone inputs. The equations for the other two output code bits are derived similarly.
- The valid output is the logical OR of all of the zone inputs.

Designing Encoders – Example

- Since all code words are used, we need a separate output to indicate when there is a valid code-word output.

```

module alarm_eqn ( output [2:0] intruder_zone,
                    output      valid,
                    input  [1:8] zone );

    assign intruder_zone[2] = zone[5] | zone[6] |
                             zone[7] | zone[8];
    assign intruder_zone[1] = zone[3] | zone[4] |
                             zone[7] | zone[8];
    assign intruder_zone[0] = zone[2] | zone[4] |
                             zone[6] | zone[8];

    assign valid = zone[1] | zone[2] | zone[3] | zone[4] |
                  zone[5] | zone[6] | zone[7] | zone[8];

endmodule

```

Designing Priority Encoders – Example

- The port list is unchanged, since we need the same inputs and outputs for the encoder. The truth table for the priority encoder is,

zone								intruder_zone			valid
(1)	(2)	(3)	(4)	(5)	(6)	(7)	(8)	(2)	(1)	(0)	
1	–	–	–	–	–	–	–	0	0	0	1
0	1	–	–	–	–	–	–	0	0	1	1
0	0	1	–	–	–	–	–	0	1	0	1
0	0	0	1	–	–	–	–	0	1	1	1
0	0	0	0	1	–	–	–	1	0	0	1
0	0	0	0	0	1	–	–	1	0	1	1
0	0	0	0	0	0	1	–	1	1	0	1
0	0	0	0	0	0	0	1	1	1	1	1
0	0	0	0	0	0	0	0	–	–	–	0

Designing Priority Encoders – Example

- Using conditional assignment:

```
module alarm_priority_1 ( output [2:0] intruder_zone,
                        output      valid,
                        input  [1:8] zone );

    assign intruder_zone = zone[1] ? 3'b000 :
                           zone[2] ? 3'b001 :
                           zone[3] ? 3'b010 :
                           zone[4] ? 3'b011 :
                           zone[5] ? 3'b100 :
                           zone[6] ? 3'b101 :
                           zone[7] ? 3'b110 :
                           zone[8] ? 3'b111 :
                           3'b000;

    assign valid = zone[1] | zone[2] | zone[3] | zone[4] |
                  zone[5] | zone[6] | zone[7] | zone[8];

endmodule
```

Designing Decoders

- Designing means deriving the Boolean equation for each output of a decoder by looking at the corresponding code word.
- Example: suppose we have an encoded 4-bit input signal (a_3, a_2, a_1, a_0), and we need to determine the Boolean equation for the output corresponding to the code word 1011.
- The output is 1 only when,

$$a_3=1, a_2=0, a_1=1 \text{ and } a_0=1$$

Thus, the output is the value of the expression = $a_3 \cdot \overline{a_2} \cdot a_1 \cdot a_0$

Designing Decoders – Example

- Many ink-jet printers have six cartridges for different coloured ink: black, cyan, magenta, yellow, light cyan and light magenta. A multibit signal in such a printer indicates selection of one of the colours. Develop a Verilog model for a decoder for use in this inkjet printer.
- Soln: The decoder has three input bits representing the choice of colour cartridge and six output bits, one to select each cartridge.

Designing Decoders – Example

- Many ink-jet printers have six cartridges for different coloured ink: black, cyan, magenta, yellow, light cyan and light magenta. A multibit signal in such a printer indicates selection of one of the colours. Develop a Verilog model for a decoder for use in this inkjet printer. The decoder has three input bits representing the choice of colour cartridge and six output bits, one to select each cartridge.

Solution:

Color	Codeword (c_2, c_1, c_0)
black	0, 0, 1
cyan	0, 1, 0
magenta	0, 1, 1
yellow	1, 0, 0
red	1, 0, 1
blue	1, 1, 0

Designing Decoders – Example

```
module ink_jet_decoder
    ( output black, cyan, magenta, yellow,
      light_cyan, light_magenta,
      input color2, color1, color0 );

    assign black      = ~color2 & ~color1 & color0;
    assign cyan       = ~color2 & color1 & ~color0;
    assign magenta    = ~color2 & color1 & color0;
    assign yellow     = color2 & ~color1 & ~color0;
    assign light_cyan = color2 & ~color1 & color0;
    assign light_magenta = color2 & color1 & ~color0;

endmodule
```