

ASSESSMENT - 2

COMBINATIONAL LOGIC - SOLUTIONS

1. A majority function is generated in a combinational circuit, where the output is equal to 1 if the input variables have more 1's than 0's otherwise the output is 0. Design a three-input majority function. (2)

Ans:

TT - 1

Eqn and kmap 1


A	B	C	Y
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

BC	00	01	11	10
A 0	0	0	1	0
A 1	0	1	1	1

$$Y = AB + AC + BC$$

2. Implement $y = AB + CD$ using NAND gates (1)


Ans:

 

$$\begin{aligned} y &= AB + CD \\ &= \overline{\overline{AB + CD}} \\ &= \overline{\overline{AB} \cdot \overline{CD}} \end{aligned}$$

3. Draw the logic diagram of a 2-to-4-line decoder with only NOR gates. Include an enable input. (2)





Ans:

 

4. Simplify the following Boolean functions using three-variable maps. (2)

- $F(x,y,z) = \Sigma(0, 1, 5, 7)$
- $F(x,y,z) = \Sigma(1, 2, 3, 6, 7)$
- $F(x,y,z) = \Sigma(3, 5, 6, 7)$
- $F(x,y,z) = \Sigma(0, 2, 3, 4, 6)$

Ans:

    

5. Prove De Morgan's theorem (2)

Ans:

- 1st theorem

$$\overline{(X+Y)} = X' \cdot Y'$$

Proof :

if $X = 0$ and $Y = 0$

$$\text{LHS } \overline{(X+Y)} = \overline{(0+0)} = \overline{(0)} = 1$$

$$\text{RHS } X' \cdot Y'$$

$$= \overline{0} \cdot \overline{0} = 1 \cdot 1 = 1$$

if $X = 1$ and $Y = 1$

$$\text{LHS } \overline{(X+Y)} = \overline{(1+1)} = \overline{(1)} = 0$$

$$\text{RHS } \bar{X} \cdot \bar{Y}$$

$$= \bar{1} \cdot \bar{1} = 0 \cdot 0 = 0$$

b) 2nd theorem

$$\overline{(X \cdot Y)} = \bar{X} + \bar{Y}$$

Proof :

if $X = 0$ and $Y = 0$

$$\text{LHS } \overline{(X \cdot Y)}$$

$$= \overline{(0 \cdot 0)} = \overline{(0)} = 1$$

$$\text{RHS } \bar{X} + \bar{Y}$$

$$= 0' + 0' = 1 + 1 = 1$$

if $X = 1$ and $Y = 1$

$$\text{LHS } \overline{(X \cdot Y)}$$

$$= \overline{(1 \cdot 1)} = \overline{(1)} = 0$$

$$\text{RHS } \bar{X} + \bar{Y}$$

$$= \bar{1} + \bar{1} = 0 + 0 = 0$$


6. Design $A + B' + C$ using 3 input and 2 input NAND gates (2)

Ans:



7. Design an XOR gate using a minimum number of NOR gates. (1)

Ans:

 

8. Simplify $ABC + AB'C + ABC'$ using

a. boolean laws

b. using K-map.

Will the simplified expression be the same or different? (3)

Ans:

a.

$$ABC + AB'C + ABC'$$

$$= AC(B + B') + ABC'$$

$$= AC + ABC'$$

$$= A(C + C'B)$$

$$= A(C + B)$$

$$= AB + AC$$

b.


A \ BC	00	01	11	10
0	0	0	0	0
1	0	1	1	1

$$F = AB + AC$$

The simplified expressions will be same for both methods

9. Design a NOR gate using only MUX. (1)


Ans:

 

10. Provide CMOS representation of a NOR gate (2)

Ans:

NOR Gate

 

Truth Table

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

11. How many select lines will there be for a 128x1 MUX? (1)

Ans:


7 select lines ($2^n = \text{number of inputs}$, where n is number of select lines)

12. How can you make an XOR gate to (2)


- behave as a buffer?
- behave as an inverter?

Ans:

a.

 


b.

 


13. How will you obtain a Half subtractor using a Half adder block without modifying the internal circuit of the block? (2)

Ans:

 


14. Design 8x1 MUX using only 4X1 MUX (3)

Ans:

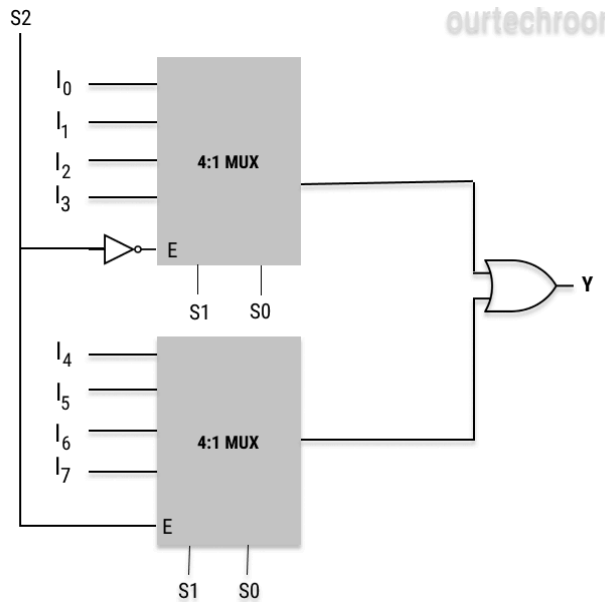

 15. Obtain the simplified output expression for the below circuit. (3)



Ans:

$$(((BC)'B) \text{ XOR } (BC)) + (A'(BC)'B)'$$

$$(((B'+C')B) \text{ XOR } (BC)) + (A'(B'+C')B)'$$

$$(BC' \text{ XOR } BC) + (A'BC')'$$

$$((BC')'BC + (BC)'(BC')) + A + B' + C$$


$$((B'+C)BC + (B'+C')(BC')) + A + B' + C$$

$$BC + BC' + A + B' + C$$

$$B + A + B' + C$$

$$=1$$

 16. Find the output expression(Q), represent Q in canonical form and obtain the POS (2)



Ans:

$$(A+B)' + BC$$

$$A'B' + BC$$

$$A'B'C + A'B'C' + ABC + A'BC$$


A \ BC	BC			
	00	01	11	10
0	1	1	1	0
1	0	0	1	0

$$F = (A+B)(B'+C)$$

17. Implement the following expression using a 3 to 8 Decoder


$$F = \sum m(0, 4, 6, 7) \text{ (2)}$$

Ans:

 


18. Design a 4 bit adder/subtractor(Block diagram). If Carry_in signal is 1, it should perform 4 bit subtraction and if it is 0, it should perform 4 bit addition (3)


Ans:

 

 19. Write the truth table for below waveform(a, b, c are inputs and y is the output) and identify the circuit (2)




Ans:

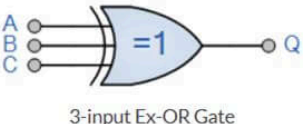Symbol	Truth Table			
 <p>3-input Ex-OR Gate</p>	C	B	A	Q
	0	0	0	0
	0	0	1	1
	0	1	0	1
	0	1	1	0
	1	0	0	1
	1	0	1	0
	1	1	0	0
	1	1	1	1
Boolean Expression $Q = A \oplus B \oplus C$		"Any ODD Number of Inputs" gives Q		

20. Consider the 2-bit multiplexer (MUX) shown in the figure. What should be the values for A₀, A₁, A₂ and A₃ for the OUTPUT to be the (2)

- XOR of C and D
- XNOR of C and D

 

Ans:

$$\text{OUTPUT} = C'D'A_0 + C'DA_1 + CD'A_2 + CDA_3$$

- If $A_0 = 0, A_1 = 1, A_2 = 1, A_3 = 0$ then $\text{OUTPUT} = C'D + CD' = C \text{ XOR } D$
- If $A_0 = 1, A_1 = 0, A_2 = 0, A_3 = 1$ then $\text{OUTPUT} = C'D' + CD = C \text{ XNOR } D$